

Experiment 4: To determine the capacitance of a capacitor using the time constant.

In this experiment you are to determine a capacitance by measuring the time constant of RC circuits. Record all observations and deductions in the spaces provided on page 8.

- (a) Connect the circuit shown in Fig. 2.1 using a $10\text{ k}\Omega$ resistor for R. Make sure that both switches are open.

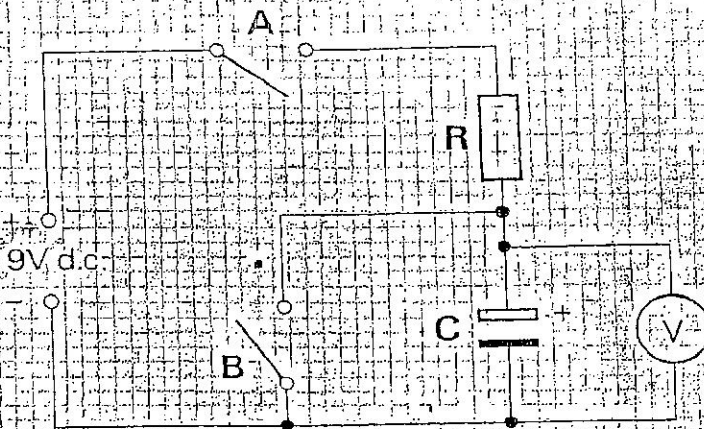


Fig. 2.1

Close switch A and wait for the voltmeter reading to reach V_0 , its maximum value. Record V_0 and the value of S where $S = 0.632 V_0$.

Open A and close B to discharge the capacitor.

- (b) The time constant τ of the circuit is equal to the time taken for the voltage to reach S after switch A is closed with the capacitor initially discharged and switch B open. Measure the time constant of the circuit as accurately as you can.

- (c) Replace the $10\text{ k}\Omega$ resistor with one of the other resistors and determine the new value for τ . Repeat the procedure until you have values of the time constant for circuits containing each of the resistors provided.

Tabulate all your values of τ and R , the value of the resistance used.

- (d) Use the grid on page 9 to plot a graph of τ/s (y-axis) against $R/\text{k}\Omega$ (x-axis).

Given that $\tau = RC$, use the graph to obtain a value for C , the capacitance of C.

- (e) The resistance values are quoted to a tolerance of 1%. State a range of values in which the true value of capacitance might lie. Show how you arrived at your answer.